

Name _____ Period _____

Physics Circuits Quiz 5

Determine the current and remaining voltage at each point.

