

Name \_\_\_\_\_ Period \_\_\_\_\_

### Circuits Quiz 2

1. Draw a circuit with one battery (cells in series), one resistor, an ammeter to measure current and a volt meter to measure electric potential difference.

2. Complete the table

<b>Quantity</b>	<b>Symbol</b>	<b>Metric Unit</b>
current		
resistance		
electromotive force		
electric potential difference		