Name _____ Period _____

Daily Quiz

Circuits #7

1. What is the resistance of a 60 watt bulb connected to a 120 volt circuit?

2. What will be the power of that same bulb (the same resistance – why?) connected to a 12 volt car battery instead?